

designideas

READERS SOLVE DESIGN PROBLEMS

Ultralow-cost, two-digit counter features few components

Noureddine Benabadji,
University of Sciences and Technology, Oran, Algeria

The ultralow-cost, two-digit-counter circuit in **Figure 1** represents an attempt to reduce the number of components using a mostly software approach and a low-cost microcontroller, the PIC16F84A. The circuit lacks the current-limiting resistors that normally connect to a seven-segment LED display's pins because a software routine lights only one of the display's segments at a time, first in the 10s display and then in the units display. Doing so keeps the circuit's maximum current consumption at a nearly constant level, even if you add a third LED display to implement a three-digit counter. The circuit also lacks digit-selection switching transistors that clas-

sic multiplexed circuits' switching transistors typically use, and the circuit includes one common-cathode and one common-anode display. The reason for this approach is that each of the microprocessor's I/O Port A and Port B lines can assume one of three states: high, low, and floating—that is, high impedance. Programming a line as an input places it in a high-impedance state, which turns the display off.

In addition, the program drives only one segment at a time and executes the following sequence: To drive the 10s display, program the line RB0 output and drive it high to light the corresponding segment of the common-cathode display and then program RB0

DIs Inside

70 Two-wire, four-by-four-key keyboard interface saves power

74 Gain-of-three amplifier requires no external resistors

► What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to edndesignideas@reedbusiness.com.

as an input. Repeat this procedure for lines RB1 through RB6. To drive the units display, repeat the process while applying a low output from RB0 to drive the common-anode display. **Figure 2** shows the circuit's timing diagram. The prototype display uses Kingbright's (www.kingbright.com) SC52-11EWA (DS₁) and SA52-11EWA (DS₂) high-efficiency, seven-segment displays that emit 2000 to 5600 μcd at a forward current of 10 mA. At a forward current of approximately 5 mA, the displays remain readable.

Early motion pictures displayed at an 18-Hz rate, which produces marginal flicker. The software executes at a rate of 180 Hz, or 10 times the minimum flicker rate. Each of the display's seven segments must illuminate for an interval of $1/(180 \times 7)$ sec, or approximately 0.8 msec. To simplify the timing routine (section Delay3 of **Listing 1**, available at www.edn.com/060817di1), the software uses a refresh interval of 1 msec.

Although this approach provides adequate segment-drive current, the display's internal LEDs carry a 3V maximum reverse-voltage rating. Driving any I/O line high applies forward bias to one segment of the common-cathode digit but applies reverse bias to the

 


Figure 1 This low-cost, two-digit counter uses few components.

corresponding segment of the common-anode display. The 16F84A requires a minimum of 2V for operation,

and thus the circuit must operate in a 2 to 3V power-supply range. The assembler source code in **Listing 1** counts

from 0 to 99 sec and serves as an unoptimized proof-of-concept software test bed for the display. [EDN](#)

 


Figure 2 The timing diagram illustrates segment- and digit-drive intervals.

Two-wire, four-by-four-key keyboard interface saves power

Stefano Salvatori, University of Rome, Rome, Italy, and Gabriele Di Nucci, EngSistemi, Rome, Italy

 You can use a microcontroller that includes an ADC to design a two-wire-plus-ground keyboard interface. For example, you can use a resistive voltage divider to identify a pressed key (**Reference 1**). A microcontroller's integrated ADC typically presents an input resistance on the order of hundreds of kilohms, and, for adequate accuracy, its keypad divider

should comprise relatively low-value resistors of 10s of kilohms. However, in battery-powered systems, a resistive divider can consume a few hundred microamperes, forcing a designer to choose an alternative classic digital-matrix array of switches and multiple I/O lines. Moreover, portable-equipment designs typically place constraints on the number of components.

To satisfy both requirements, the circuit in **Figure 1** uses a matrix keypad and a resistor network divided into two row and column sections. For the four-by-four-key keypad, seven resistors are sufficient to encode any pressed key, and the circuit consumes power only while a key remains closed. Conversely, with no keys pressed, the standby current approaches zero. Using only two values of resistors, let $R_A = R_B = R_C = R_1$ and $R_D = R_E = R_F = R_G = R_2$. Assigning values from zero to three for the keys' x and y addresses, you can calculate the voltage across resistor R_G for any key closure by solving the following **equation**:

 


Figure 1 A two-wire resistive voltage-divider interface encodes a four-row-by-four-column keypad.

 


Figure 2 Using the microcontroller's analog reference-voltage output and ratiometric analog-to-digital conversion ensures correct encoding of the keypad.

TABLE 1 SINGLE-KEY OUTPUT CODES

		Keys pressed/resistance (Ω)			
		X			
		3	2	1	0
Y	3	1/ 15 to 16	2/ 21	3/ 32	A/ 63 to 64
	2	4/ 17	5/ 23	6/ 36	B/ 85
	1	7/ 18	8/ 25	9/ 42	C/ 127
	0	*/ 19	#/ 28	#/ 51	D/ 255

Note: The figures preceding the slashes represent the keypad's key labels.

$$V(x,y) = V_{REF} \times \frac{R_2}{x \times R_1 + y \times R_2 + R_2}$$

Driving the resistor array from V_{REF} , the ADC's reference voltage, allows you to perform a ratiometric conversion that eliminates errors in key encoding due to fluctuations in V_{REF} . The following equation describes the voltage-division ratio, $r(x,y)$, for any keystroke.

$$r(x,y) = \frac{V(x,y)}{V_{REF}} = \frac{1}{(1 + x \times p + y)}$$

The ratio $p = R_1/R_2$ represents the ratio between row- and column-group resistors' values. For $p=4$, you calculate 16 values of $r(x,y)$, in the $[1/16, 1]$ range, as a function of the pressed key's position. In general, the minimum difference between r partitioning ratios

occurs for the nearest keys as the (3,2) and (3,3) x,y indexes indicate. For an N -bit ADC and a ratio of $p=4$, the ADC should have a resolution that satisfies the following equation: $2^{-N} < r(3,2) - r(3,3) = 15^{-1} - 16^{-1} = 240^{-1}$. Note that the reciprocal of 240 (0.0041...) exceeds the reciprocal of 2^8 , and the circuit thus requires an ADC capable of at least 8-bit resolution ($N \geq 8$ bits).

Unfortunately, standard-value components with nominal tolerance, T , cannot provide an ideal solution to this equation. Instead, you calculate a partitioning-ratio difference, $d = r(3,2) - r(3,3)$, for the worst-case condition. The lowest value of d occurs for a minimum value of R_C and R_D and the maximum value of R_A , R_B , R_C , R_E , and R_F . You can account for all the resistors' values and define a generic ratio, p , for

TABLE 2 TWO-KEY OUTPUT CODES

Keys pressed	Resistance (Ω)
C+#	141 to 142
C+0	134 to 135
C+*	132
B+#	109
B+0	98
B+9	91
B+8	88
A+8	76
A+7	70 to 71
A+6	68

the nominal values of R_1 and R_2 :

$$d_{MIN}(p,T) = (1-T)^2 / \{ [3 \times (p+1) + (3p+1) \times T] \times [(3p+4) + 3 \times p \times T] \} > 2^{-N}$$

The same value of T applies to all resistors. If $n=8$ and $p=4$, the previous equation yields a solution of $T < 0.018$, which indicates that resistors of $\pm 1\%$ tolerance correctly encode 16 keys. Moreover, if you now impose the chosen fixed tolerance, T , you can solve the equation to obtain the required limit on the p ratio between the values of R_1 and R_2 . If $T=0.01$, the solution to the equation becomes $p < 4.074$.

The circuit in Figure 2 uses Freescale's (www.freescale.com) Nitron MC68HC908QT4 microprocessor, which serves as a test bed for a keypad based on the above-calculated values, and uses pow-

er-supply voltage V_{CC} as the resistor matrix's reference voltage, V_{REF} . To satisfy the requirement for $p(4.074 > p > 4)$, use $R_1 = 10 \text{ k}\Omega \pm 1\%$ tolerance and $R_2 = 40.2 \text{ k}\Omega \pm 1\%$ tolerance, both standard values that the E48 series offers. **Table 1** lists output codes corresponding to 16 individually pressed keys, and **Table 2** lists data obtained when simultaneously pressing two keys and illustrates that two-key combinations can evoke special functions.

If your application requires a microcontroller that lacks an internal inter-

rupt that the ADC generates, you can connect an external comparator to the output voltage in **Figure 1**. Set the comparator's threshold lower than the lowest voltage developed at the output voltage—approximately V_{REF} divided by 16 in the example—and the comparator's output serves as a keypad-interrupt source for the microcontroller.

Note that a microcontroller with a 10-bit ADC, such as a Freescale MC68HC908QB or a Texas Instruments (www.ti.com) MSP430F11 can service a five-row by six-column keypad

matrix encoded by 10 resistors. Repeating the analysis shows that a row-to-column p ratio of 5 to 5.51 and a required resistor tolerance of less than 4.3% correctly encode the keys. You can use values of $10 \text{ k}\Omega$ for R_1 and $51.1 \text{ k}\Omega$ or $53.6 \text{ k}\Omega$ for R_2 of the $\pm 1\%$ -tolerance E48 series.

REFERENCE

Amorim, Vitor, and J Simões, "ADC circuit optimizes key encoding," *EDN*, Feb 4, 1999, pg 101, www.edn.com/article/CA56657.

Gain-of-three amplifier requires no external resistors

Marián Štofka, Slovak University of Technology, Bratislava, Slovakia



Analog Devices' ADA4862-3 comprises three wideband am-

plifiers, each configured by an internal, fixed-value resistive-feedback network

as a noninverting gain-of-two amplifier. Due to its internal feedback networks, the device offers a bandwidth of 300 MHz and excellent insensitivity to stray capacitance, variations in pc-board layout, and proximity of other devices. According to its specifications, each of IC_1 's three internal amplifiers offers

 


Figure 1 A one-IC amplifier with a voltage gain of three provides flat response to more than 60 MHz.

three gain configurations—two, one, or negative one (**Reference 1**). When you configure it for a gain of two, a cascade of two or three amplifiers yields gains of four or eight, respectively. If your application requires a gain of three, you can use the circuit in **Figure 1**. Amplifier A_3 serves as an impedance converter with a net voltage gain of one and a low-impedance driver for A_1 's gain-setting network. Amplifier A_2 provides a gain of two at its noninverting input.

In addition, A_3 introduces the proper time delay (phase shift) in A_1 's inverting-input path and thus roughly equalizes the time delay in A_1 's noninverting signal path. This configuration improves the circuit's dynamic performance over that you can achieve when A_1 's inverting input connects directly to the input signal. A 4.7-pF chip capacitor that connects from voltage follower A_3 's output to ground

MORE AT EDN.COM

+ For more Design Ideas, visit www.edn.com/designideas.

+ For our best entries, go to www.edn.com/bestofdesignideas.

reduces the voltage follower's output impedance at frequencies of 100 MHz and above to ensure A_1 's stability.

If you configure it as a differential amplifier, A_1 amplifies the input signal by a factor of two at its noninverting input and by a factor of negative one at its inverting input. The final voltage at A_1 's output comprises the algebraic sum of both components: $V_{OUT} = 4 \times V_{IN} - V_{IN} = 3 \times V_{IN}$. In a conventional voltage amplifier, reducing negative feedback increases the overall gain. In contrast, cascading amplifiers with negative-voltage-feedback networks only slightly

reduces the circuit's bandwidth. The net gain decrease at a frequency of 65 MHz amounts to 0.1 dB, or approximately 1.15% of a single gain-of-two amplifier's dc gain. For the gain-of-three amplifier in **Figure 1**, the gain decrease at 65 MHz amounts to approximately 2.3% of the circuit's dc gain.

For the best high-frequency performance, connect the ADA4862's internal amplifiers as **Figure 1** shows to minimize the lengths of the device's external interconnections. You can cascade additional ADA4862-3 ICs to produce any gain expressed as $3^M \times 2^N$, where M and N represent integers, including zero—that is, gains of six, nine, 12, and so on.EDN

REFERENCE

■ ADA4862-3 data sheet, Analog Devices Inc, www.analog.com/UploadedFiles/Data_Sheets/360747397ADA4862_3_a.pdf.